

## Problem 2

Find the capacitor voltage  $v_c(t)$ . Note that the two sources have non-identical frequencies.

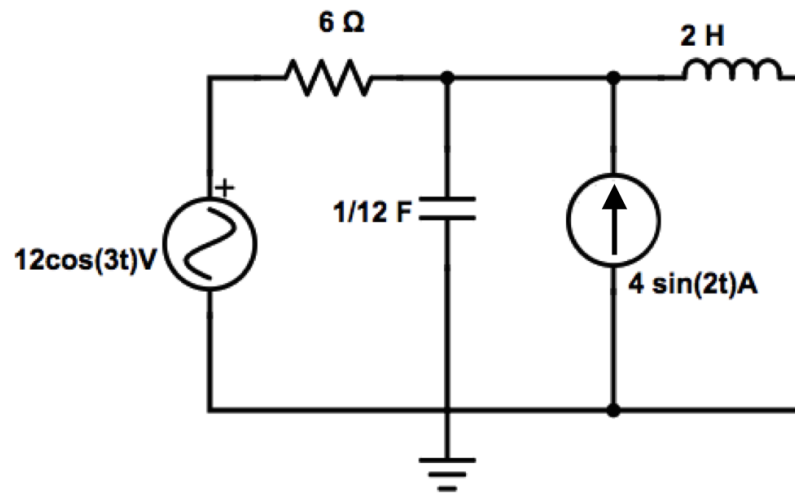


Figure 2