

# ECE 10C

## Homework 6

### Due: Tuesday 6/4 at 4:00 pm

Please print out all the worksheets (including this cover page).  
Make sure to securely staple all the worksheets together.

Full Name:

---

ID number:

---

Number of pages attached:  
(excluding cover page)

---

Name of lab TA:

### Problem 1

For the circuit in Fig. 1

1. What type of filter is this? Plot the gain if  $R = L = C = 1$ .
2. For what values of  $R$  is the circuit resonant?
3. Given the type of filter, specify whether you would like this circuit to be resonant with high  $Q$  or not.

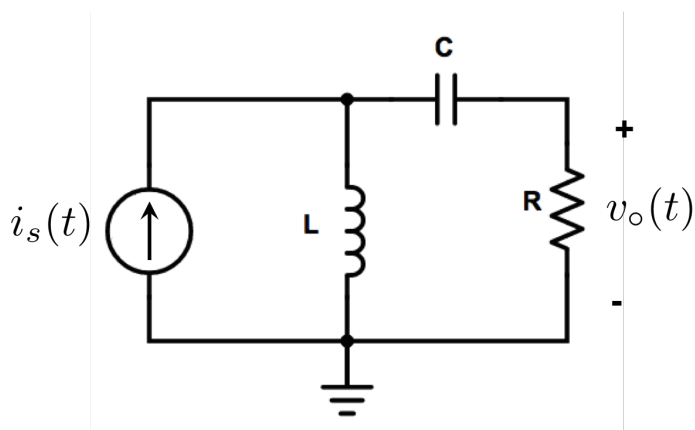


Figure 1

## Problem 2

Consider the following circuit.


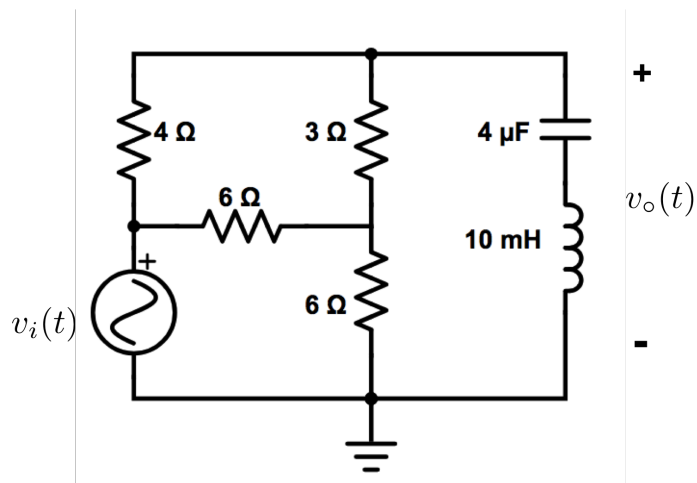


Figure 2

1. Determine the filter type and specify its parameters (e.g., center frequency and bandwidth).


Problem 2 - continued

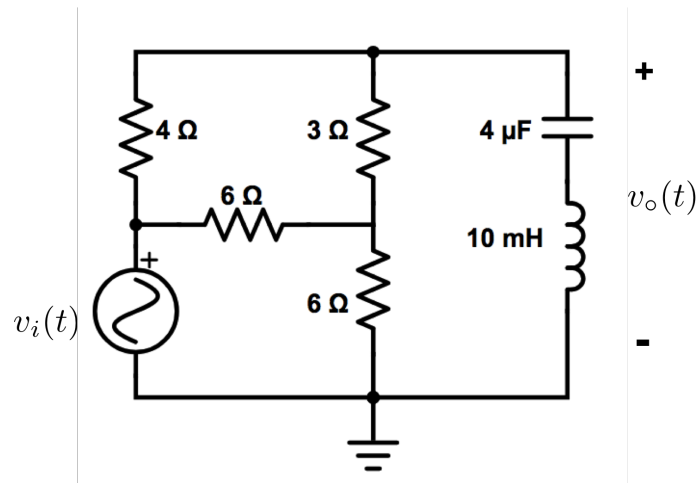

2. Determine the average power dissipated by the circuit if  $v_i(t) = 200 \sin(5000t)$ .

### Problem 3

We would like to build an AM radio receiver using a **series RLC circuit** working as a bandpass filter. We have decided to use a  $240\ \mu\text{H}$  inductor with an internal resistance of  $12\ \Omega$ , and a variable capacitor whose capacitance varies between 40 to 360 pF. A radio “tunes” into a certain frequency by adjusting its receiver circuit so that it resonates at that frequency, and it only catches that specific frequency.

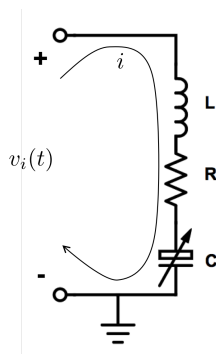


**Figure 3:** AM radio receiver

1. Determine the range of channel frequencies that we can tune into with this receiver;
2. Determine the receiver's bandwidth;

### Problem 3 - continued

3. AM radio broadcasting has assigned channels, ranging from 540 kHz to 1,700 kHz and spaced at 10-kHz intervals. What is the largest value of the internal resistance that would allow us to avoid adjacent channel interference (i.e., listening to more than one channel at once)?

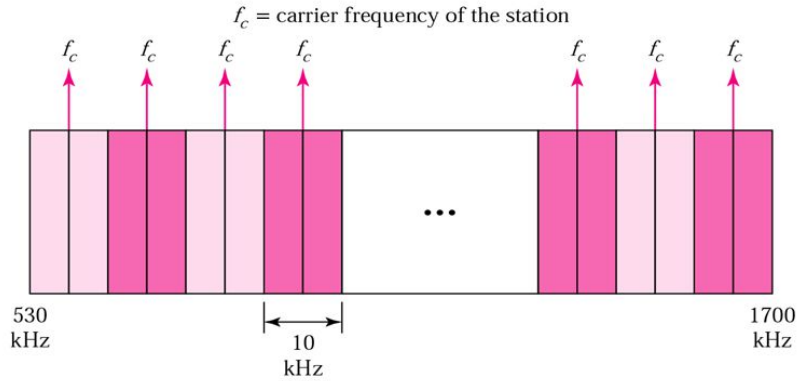

**Figure 4:** AM radio band

(For simplicity, assume that the bandwidth of the RLC circuit is symmetric around the resonance frequency)