

Problem 2

Find the value of R that leads to a critically damped response.

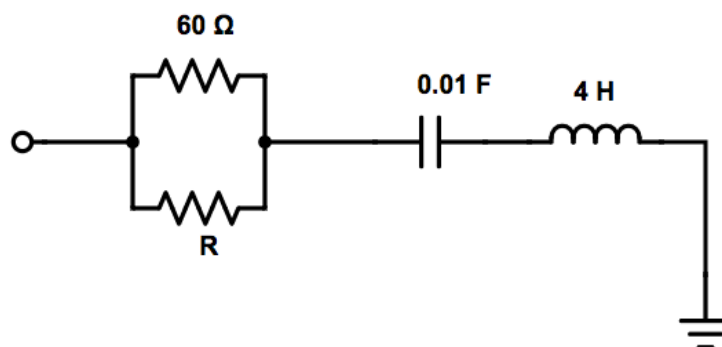


Figure 2