Problem 2

Using the impedance method, find v(t) and i(t). Give a brief explanation of every step to reach the solution.

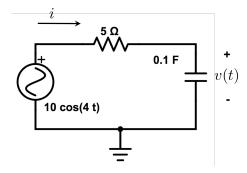


Figure 1