

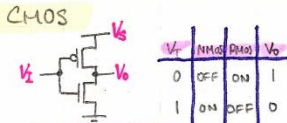


Inverter circuits - triode (MOSFET)

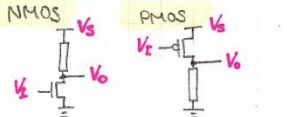

Transfer Curve

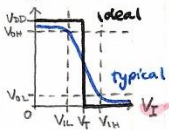

$$V_T = V_{TN} + \sqrt{\frac{K_p}{K_n}} (V_S + V_{TP})$$

When $I_{DN} = I_{DP}$

Unified Model

NMOS $V_T > 0$

$$i_{DS} = \begin{cases} 0 & V_{GS} < V_T \\ \frac{K}{2} (V_{GS} - V_T)^2 & V_{GS} \geq V_T \end{cases}$$

$V_{GS} < V_T$ Cutoff
 $V_{GS} \geq V_T$ Triode
 $V_{GS} \geq V_T$ Saturation

PMOS $V_T < 0$

$$i_{SD} = \begin{cases} 0 & V_{GS} < |V_T| \\ \frac{K}{2} (V_{GS} - |V_T|)^2 & V_{GS} \geq |V_T| \end{cases}$$

$V_{GS} < |V_T|$ Cutoff
 $V_{GS} \geq |V_T|$ Triode
 $V_{GS} \geq |V_T|$ Saturation

$$K = \mu C_{ox} \frac{W}{L}$$

$$K = \mu C_{ox}$$

SR Model

$$i_D = \frac{V_{GS}}{R_{on}} \quad R_{on} = R_{ch} \frac{L}{W}$$

under triode conditions

set $\begin{cases} \mu = \text{mobility} \\ C_{ox} = \text{capacitance per area of gate oxide} \\ W = \text{MOSFET width} \\ L = \text{MOSFET length} \end{cases}$

N MOSFETs in parallel
 ↳ Act as 1 MOSFET w/ dimensions K_n
 ↳ $K_n = N K_0$
 K_0 - dimensions of 1
 ↳ allows for greater I

Diode connected MOSFET




Always in saturation: $V_{DS} = V_{GS}$
 Small signal: $r_{DS} = \frac{V_{GS}}{g_m V_{GS}} = \frac{1}{g_m}$

Amplifiers - saturation (MOSFET)


Common Source




Common drain

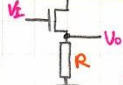


MOSFET transfer curve

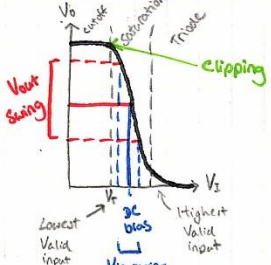

IV Curve

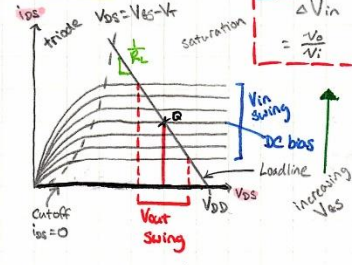


Clipping - amp operates partly in cutoff

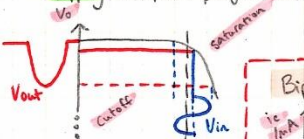

Highest Valid Input



$$V_{in,max} = -1 + \sqrt{1 + 2V_{DS} R_L K}$$

Bipolar Junction Transistor

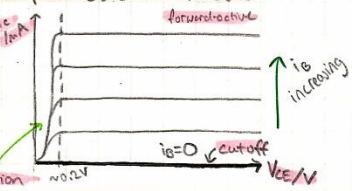


Mode	E-B Junction	C-B Junction
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Saturation	Forward	Forward

Equivalent circuit

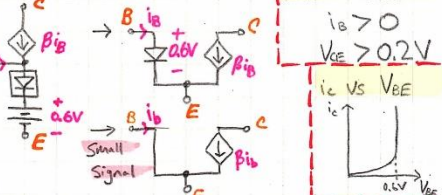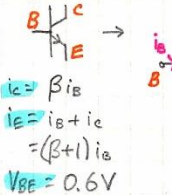

Amplifiers (BJT)

Common Emitter

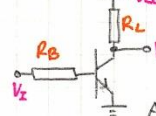


$$i_B = \frac{V_i - 0.6}{R_B}$$

$$i_E = \beta i_B$$


$$i_C = (\beta + 1) i_B$$

$$V_O = V_{CC} - i_C R_L = V_{CC} - \beta \frac{R_L}{R_B} (V_i - 0.6)$$

Common Collector

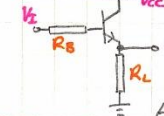

$$A \approx 1$$

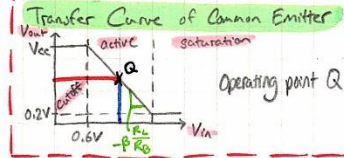

Linear Taylor series expansion

$$y = f(x_0) + \left. \frac{df}{dx} \right|_{x_0} (x - x_0)$$

$$i_D = \frac{K}{2} (V_{GS} - V_T)^2 + K (V_{GS} - V_T) V_{GS}$$

Small Signal Analysis

MOSFET

$$V_{GS} = V_{GS} + v_{gs}$$

$$i_D = I_D + i_d$$

total DC AC/SS

$$i_d = K (V_{GS} - V_T) v_i = g_m v_i$$

$$g_m = \text{transconductance} = K (V_{GS} - V_T)$$

Input/Output Resistance (SS)

↳ set independent V_i, I_i source's = 0
 ↳ Use SS model → apply r_{DS} at input/output
 $r = \frac{V_{DS}}{I_{DS}}$

MOSFET amplifier - common source

$$r_i \approx \infty \quad r_o = R_L$$

MOSFET amplifier - common drain

$$r_i \approx \infty \quad r_o \approx \frac{1}{g_m}$$

BJT amplifier - common emitter

$$r_i = R_B \quad r_o = R_L$$


BJT amplifier - common collector

$$r_i = R_B + (\beta + 1) R_E \quad r_o \approx \frac{R_E}{\beta + 1}$$


Equivalent Models

Component	Large signal	Small signal
MOSFET		
Resistor		
Vsource		
I source		
Capacitor		
Inductor		
Block		
Box		
Block Box		

Differential Amplifier

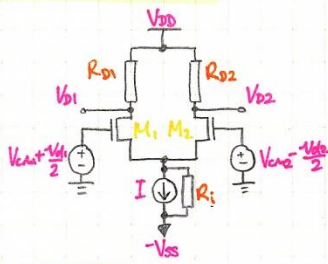

Small Signal
Common Mode

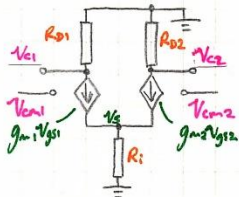

If $R_{D1} = R_{D2} = R_D$, $g_{m1} = g_{m2} = g_m$, $V_{gs1} = V_{gs2} = V_{gs}$, $V_{d1} = V_{d2} = V_d$

Common Mode

$$g_m V_{gs} + g_m V_{gs} = \frac{V_d}{R_i}$$

$$* V_{gs} = \frac{1}{2g_m R_i + 1} V_{cm}$$

If R_i large, $2g_m R_i \gg 1$
 $V_{gs} \approx \frac{1}{2g_m R_i} V_{cm}$

$$g_m V_{gs} = \frac{1}{2R_i} V_{cm}$$

$$V_{d1} = V_{d2} = -\frac{R_D V_{cm}}{2R_i}$$

$$V_{co} = V_{d1} - V_{d2} = 0$$

$$A_c = 0$$

If symmetrical EXCEPT $R_{D1} = R_D$, $R_{D2} = R_D + \Delta R_D$

Common Mode

$$* V_{gs} = \frac{1}{2g_m R_i + 1} V_{cm}$$

$$g_m V_{gs} = \frac{g_m}{2g_m R_i + 1} V_{cm}$$

$$V_{d1} = -\frac{g_m R_D}{2g_m R_i + 1} V_{cm}$$

$$V_{d2} = -\frac{g_m (R_D + \Delta R_D)}{2g_m R_i + 1} V_{cm}$$

$$V_{co} = V_{d1} - V_{d2} = -\frac{g_m \Delta R_D}{2g_m R_i + 1} V_{cm}$$

$$A_c = \frac{V_{co}}{V_{cm}} = -\frac{g_m \Delta R_D}{2g_m R_i + 1}$$


Operational Amplifiers (OP-amps)

$$V_o = A(V^+ - V^-)$$

ideal: $A = \infty$, $r_{out} = 0$
 $i^+ = i^- = 0$, $r_{in} = \infty$
 $V^+ - V^- = 0$ (virtual short)

Negative feedback \rightarrow output signal fed back into input

Non-inverting op-amp

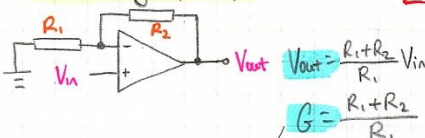

$$V_{out} = \frac{R_1 + R_2}{R_1} V_{in}$$

$$G = \frac{R_1 + R_2}{R_1}$$

Common-mode rejection ratio (CMRR)

$$CMRR = \frac{A_d}{A_c}$$

A_d - Difference mode gain
 A_c - Common mode gain


Difference mode signal

$$V_{do} = V_{d1} - V_{d2}$$

Common mode signal

$$V_{co} = \frac{V_{d1} + V_{d2}}{2}$$

Difference Mode

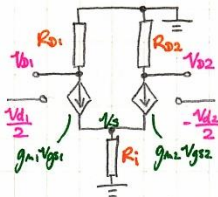

Difference Mode

$$g_m V_{gs1} + g_m V_{gs2} = \frac{V_d}{R_i}$$

$$g_m \left(\frac{V_{d1}}{2} - V_s \right) + g_m \left(\frac{V_{d2}}{2} - V_s \right) = \frac{V_d}{R_i}$$

$$-2g_m V_s = \frac{V_d}{R_i}$$

* g_m independent from R_i so $V_s = 0$

$$V_{d1} = -\frac{g_m R_D V_d}{2}$$

$$V_{d2} = \frac{g_m R_D V_d}{2}$$

$$V_{do} = V_{d1} - V_{d2} = -g_m R_D V_d$$

$$A_d = \frac{V_{do}}{V_d} = -g_m R_D$$

Difference Mode

$$* V_s = 0$$

$$V_{d1} = -\frac{g_m V_d R_D}{2}$$

$$V_{d2} = \frac{g_m V_d (R_D + \Delta R_D)}{2}$$

$$V_{do} = V_{d1} - V_{d2}$$


$$= -g_m V_d \left(R_D + \frac{\Delta R_D}{2} \right)$$

$$A_d = \frac{V_{do}}{V_d} = -g_m \left(R_D + \frac{\Delta R_D}{2} \right)$$

$$CMRR = \frac{A_d}{A_c}$$

$$CMRR = \frac{(R_D + \frac{\Delta R_D}{2})(2g_m R_i + 1)}{\Delta R_D}$$

Inverting op-amp

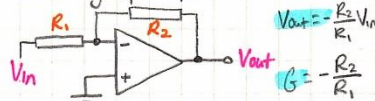

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$


$$G = -\frac{R_2}{R_1}$$

Op-amp adder






$$V_{out} = -R_3 \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

Op-amp Subtractor

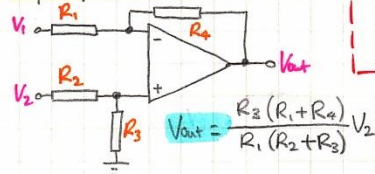
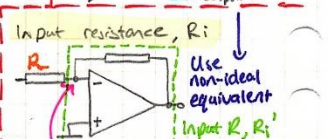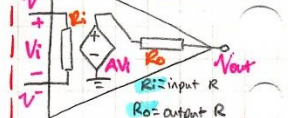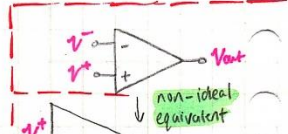
$$V_{out} = \frac{R_2(R_1 + R_4)}{R_1(R_2 + R_3)} V_2 - \frac{R_4}{R_1} V_1$$



Input resistance, R_i
 Use non-ideal equivalent
 Input R_i , R_i'
 apply V_{test} here
 $R_i = R_i' + R_-$ (series)

Op amp saturation
 $+ve: A(v^+ - v^-) > +V_{cc}$
 $-ve: A(v^+ - v^-) < -V_{cc}$

Energy Storage Elements:

Capacitors (Electrical Energy)

$$q(t) = C v(t)$$

$$i(t) = C \frac{dv(t)}{dt} \quad v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt$$

$$\text{stored energy} = W_E(t) = \frac{q^2(t)}{2C} = \frac{C v(t)^2}{2}$$

Inductors (Magnetic Energy)

$$\lambda(t) = L i(t) \text{ [Aux linkage]}$$

$$v(t) = L \frac{di(t)}{dt} \quad i(t) = \frac{1}{L} \int_{-\infty}^t v(t) dt$$

$$\text{stored energy} = W_M(t) = \frac{\lambda^2(t)}{2L} = \frac{L i(t)^2}{2}$$

Combinations:

Capacitors		Inductors	
Series	Parallel	Series	Parallel
$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = L_1 + L_2$	$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$

Capacitor

\hookrightarrow discharged \rightarrow short

\hookrightarrow fully charged \rightarrow open

\hookrightarrow $v(t)$ continuous

Inductor

\hookrightarrow discharged \rightarrow open

\hookrightarrow fully charged \rightarrow short

\hookrightarrow $i(t)$ continuous

Step functions



$$v(t) = \begin{cases} 0 & t \leq 0 \\ V_0 & t > 0 \end{cases}$$

$$v(t) = \begin{cases} 0 & t \leq 0 \\ \frac{V_0}{t} & t > 0 \end{cases}$$

$$v(t) = \begin{cases} 0 & t \leq 0 \\ V_0 & t > 0 \end{cases}$$

$$v(t) = \begin{cases} 0 & t \leq 0 \\ V_0 & t > 0 \end{cases}$$

$$v(t) = \begin{cases} 0 & t \leq 0 \\ V_0 & t > 0 \end{cases}$$

$$v(t) = \begin{cases} 0 & t \leq 0 \\ V_0 & t > 0 \end{cases}$$

Parallel Plate capacitor

$$C(t) = \frac{\epsilon A(t)}{l(t)}$$

Inductor

$$L(t) = \frac{\mu N^2 A(t)}{l(t)}$$


MOSFET Gate Capacitance

$$C_{gs} = \frac{\epsilon_{ox} L W}{d}$$

$$C_{ox} = \frac{\epsilon_{ox}}{d}$$

$$C_{gs} = C_{ox} L W$$

Transformers

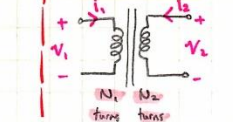

$$\frac{V_1(t)}{N_1} = \frac{V_2(t)}{N_2}$$


$$N_1 i_1(t) = -N_2 i_2(t)$$

$$N_1 i_1(t) = -N_2 i_2(t)$$

$$N_1 i_1(t) = -N_2 i_2(t)$$

$$N_1 i_1(t) = -N_2 i_2(t)$$


$$N_1 i_1(t) = -N_2 i_2(t)$$

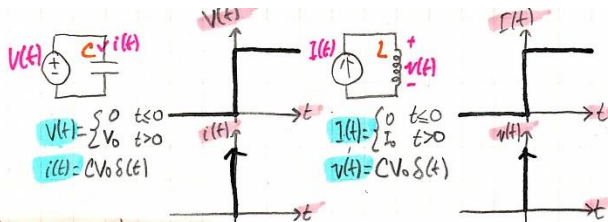

First order transients

Capacitor (RC circuit)

Step response (charging)

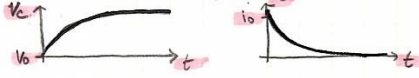

$$\text{Form: } V_c(t) = A(1 - e^{-t/\tau})$$

$$i_c(t) = B e^{-t/\tau}$$

Natural response (discharging)




$$\text{Form: } V_c(t) = A e^{-t/\tau}$$

$$i_c(t) = -B e^{-t/\tau}$$

Inductor (RL circuit)


Step response (charging)

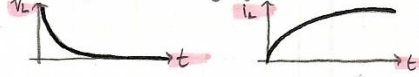

$$\text{Form: } V_c(t) = A e^{-t/\tau}$$

$$i_c(t) = B(1 - e^{-t/\tau})$$

Natural response (discharging)

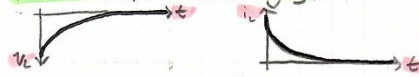

$$\text{Form: } V_c(t) = -A e^{-t/\tau}$$

$$i_c(t) = B e^{-t/\tau}$$

How to solve First order transients

- 1) Find **homogeneous solution** (natural response)
- 2) Find **particular solution** (forced/driven response)
- 3) Solution = homogeneous soln + particular soln.
- 4) Apply initial conditions
- ↳ Apply **Kirchoff's** to get differential eq.
- ↳ Set **constants = 0** → homogeneous soln.
- ↳ Sub homogeneous soln into diff eq. w/ constants
→ Method of undetermined coefficients → add unknown K
- ↳ Sub in **initial conditions**

E storage in equivalent components

If two capacitors, C_1, C_2 make C_{eq}

$$V_{c1}(t) + V_{c2}(t) = V_{ceq}(t)$$

$$V_{c1}(t) = A_1 e^{-t/\tau} + B$$

$$V_{c2}(t) = A_2 e^{-t/\tau} - B$$

$$V_{ceq} = (A_1 + A_2) e^{-t/\tau}$$

If two inductors L_1, L_2 make L_{eq}

$$i_{L1}(t) + i_{L2}(t) = i_{Leq}(t)$$

$$i_{L1}(t) = A_1 e^{-t/\tau} + B$$

$$i_{L2}(t) = A_2 e^{-t/\tau} - B$$

$$i_{Leq} = (A_1 + A_2) e^{-t/\tau}$$

If two storage elements of same type. $X_1, X_2 \rightarrow X_{eq}$

X_{eq} fully charges / discharges as $t \rightarrow \infty$

$$\frac{[E_{x1}(0) + E_{x2}(0)] - E_{x_{eq}}(0)}{\text{initial E in both elements}} = \frac{[E_{x1}(\infty) + E_{x2}(\infty)] - E_{x_{eq}}(\infty)}{\text{initial E in eq element}} = \frac{E_{\text{trapped in both elements}}}{E_{\text{trapped in both elements}}}$$

General form of equations:

Capacitor

$$V_c(t) = V_c(\infty) + [V_c(0) - V_c(\infty)] e^{-t/\tau}$$

$$V_c(t) = V_c(0) e^{-t/\tau} + V_c(\infty) (1 - e^{-t/\tau})$$

Inductor

$$i_L(t) = i_L(\infty) + [i_L(0) - i_L(\infty)] e^{-t/\tau}$$

$$i_L(t) = i_L(0) e^{-t/\tau} + i_L(\infty) (1 - e^{-t/\tau})$$

Propagation delay (gate delay)

↳ time for circuit to reliably output desired output



$t_{pd1 \rightarrow 0}$ 1→0 change at output

$t_{pd0 \rightarrow 1}$ 0→1 change at output

Rise time: 0→1 change at output

Fall time: 1→0 change at output

$$t_{pd} = \max(t_{pd1 \rightarrow 0}, t_{pd0 \rightarrow 1})$$

for multiple input/output:

input/output pair $i \rightarrow j$ t_{pd}^{ij}

$$t_{pd} = \max_i t_{pd}^{ij}$$


State Variables

$$\frac{d}{dt}(\text{state variable}) = f(\text{state variable}, \text{input variable})$$

If linear:

$$\frac{d}{dt}(\text{state variable}) = K_1(\text{state variable present value}) + K_2(\text{input variable})$$


Op Amp RC Circuits

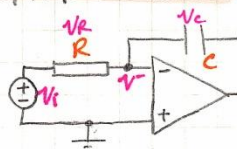

Integrator

$$V_c = -\frac{1}{RC} \int V_i dt$$
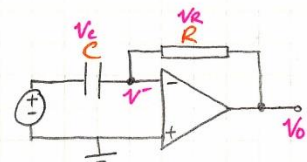
$$V_o \approx -\frac{1}{RC} \int V_i dt$$



Differentiator

$$V_c = -RC \frac{dV_i}{dt}$$


$$V_o \approx -RC \frac{dV_i}{dt}$$

Op amp positive feedback

↳ turn continuous analog signals into 2 state signals

Comparator

Non-inverting

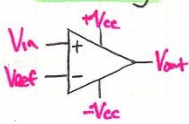


If $V_{in} > V_{ref}$

$V_{out} = +V_{cc}$

If $V_{in} < V_{ref}$

$V_{out} = -V_{cc}$

Inverting

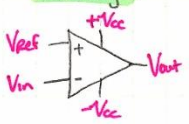



If $V_{in} > V_{ref}$

$V_{out} = -V_{cc}$

If $V_{in} < V_{ref}$

$V_{out} = +V_{cc}$

RC oscillator

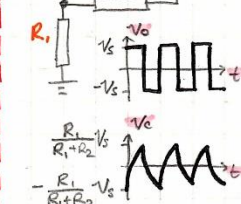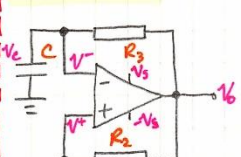

Square wave period (T) & Energy storage

If $T \approx 5\tau$

element \approx fully charges/discharges

$T \approx \tau$

element $\approx 1 - \frac{1}{e} \approx 63.2\%$ charges

or $\approx \frac{1}{e} \approx 36.8\%$ discharges


[depending on variable & element]

$T \ll \tau$


element doesn't charge, $V_0 = \text{constant}$

Inductive element ramp input


part a)

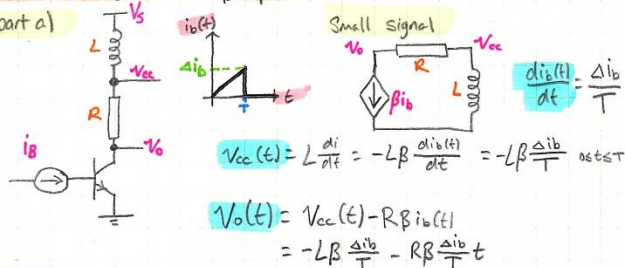

part b)

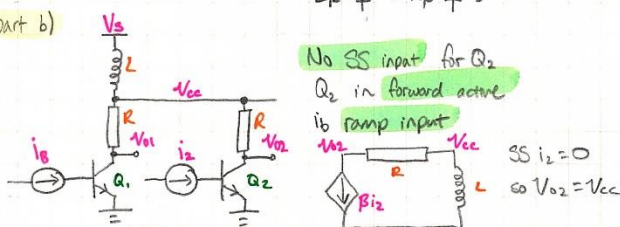


IC $L=0 \rightarrow$ no inductor

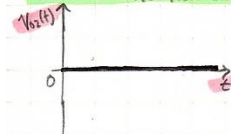



Inductor causes crosstalk between 2 amplifiers

Integrators to measure capacitance

Series RC

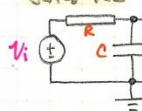

Op-amp integrator

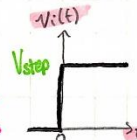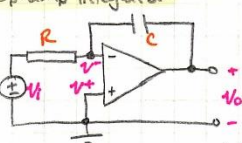

part a) V_0 for both circuits:

Series RC

$$V_0(0) = 0$$

$$V_0 = V_{step} - RC \frac{dV_0}{dt}$$

$$V_0 = V_{step} (1 - e^{-t/RC})$$

Opamp

$$V^- = V_{step} - RC \frac{d(V^- - V_0)}{dt}$$

$$V^+ = 0 \quad V^- = -\frac{V_0}{A}$$

$$-\frac{V_0}{A} = V_{step} - RC \frac{d(-\frac{V_0}{A} - V_0)}{dt}$$

$$-V_0 = AV_{step} + (1+A)RC \frac{dV_0}{dt}$$

$$V_0(t) = -AV_{step} (1 - e^{-\frac{t}{(1+A)RC}})$$

Same form

part b) $\tau_{RC} = RC$ $\tau_{opamp} = (1+A)RC$

part c) Output V_0 at $t = t_0$ (we $e^x = 1 - x + \frac{x^2}{2!} - \dots$)

Series RC

$$V_0(t) = V_{step} \frac{t}{RC}$$

$$|V_0(t)| = V_{step} \frac{t}{RC}$$

Opamp

$$V_0(t) = -AV_{step} \frac{t}{(1+A)RC}$$

$$|V_0(t)| \approx V_{step} \frac{t}{RC}$$


Equivalent

part d) Op amp integrator acts as ideal integrator over longer


period of time due to greater τ

\rightarrow easier to measure smaller C values


Equivalent Circuits

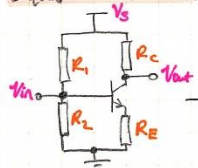


Can Thevenin's

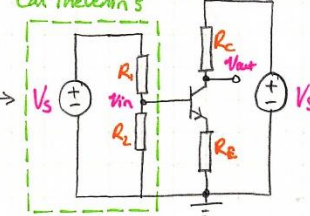


Inductive element with MOSFET inverters

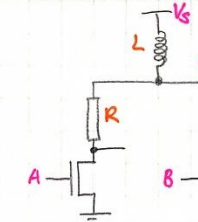

For part a)

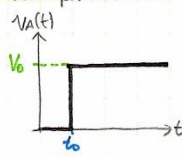

part b)

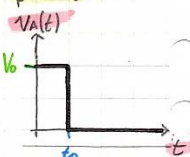

part a) $B = 0V$ constant $V_0 > V_T$, $V_S > V_T$

Eg circuit (SR Model) $t > t_0$


$$i_L(t_0) = 0, \quad i_L(\infty) = \frac{V_S}{R + R_{on}}$$

$$V_{DD} = i_L(R + R_{on})$$

$$i_L(t) = \frac{V_S}{R + R_{on}} (1 - e^{-(t-t_0)/\tau})$$

$$V_{DD}(t) = V_S (1 - e^{-(t-t_0)/\tau})$$

$V_{DD}(t) = V_0(t)$

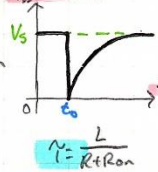

part b) $B = 5V$ constant $V_0 > V_T$, $V_S < V_T$

Eg circuit (SR Model) $t > t_0$


$$\text{before } t_0, i_L = \frac{2V_S}{R + R_{on}} = i_L(0)$$

$$i_L(0) = \frac{V_S}{R + R_{on}}$$


$$i_L(t) = \frac{V_S}{R + R_{on}} (1 + e^{-(t-t_0)/\tau})$$

$$V_{DD}(t) = V_S (1 + e^{-(t-t_0)/\tau})$$
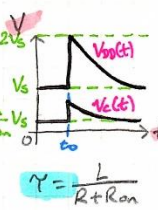
$$V_0(t) = \frac{R_{on}}{R + R_{on}} V_S (1 + e^{-(t-t_0)/\tau})$$



Energy in combinations of inductors

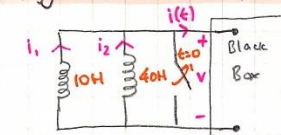

$$i_1(0) = -6A \quad i_2(0) = 10A$$

$$i_{L1} = 4e^{-1.25t}$$

Individual inductors

$$i_1(t) = 3.2e^{-1.25t} - 9.2$$

$$E \text{ delivered by } L_2 = \frac{1}{2} i_1(0)^2 - \frac{1}{2} i_1(\infty)^2 = 64J$$

Initial E in L_1 & L_2

$$E_{L1}(0) = \frac{1}{2} i_1(0)^2 = 180J$$

$$E_{L2}(0) = \frac{1}{2} i_2(0)^2 = 2000J$$

Final E in L_1 & L_2

$$E_{L1}(\infty) = 423.2J$$

$$E_{L2}(\infty) = 1692.8J$$

E trapped:

$$[E_{L1}(0) + E_{L2}(0)] - [E_{L1}(\infty) + E_{L2}(\infty)] = [E_{L1}(\infty) + E_{L2}(\infty)]$$

Initial E in L_1, L_2

\rightarrow E in eq

Final E in L_1, L_2

To solve circuits w/ multiple storage elements

1) Find equivalent component

2) Find τ (use Thevenin's) of eq component = τ of each element

3) Apply initial conditions to eq component

4) Use eq equation to solve for each element & apply initial conditions