

[**Important:** Please try your best to write your derivations clearly and briefly explain the steps. This can help you gain partial credit if you make calculation mistakes.]

**Problem 2 [40 pts]**

In the circuit in Fig. 1, the switch has been closed for all  $t < 0$ . At  $t = 0$ , the switch is opened (and remains open for  $t > 0$ ).

1. [5 pts] Find  $v(0)$  and  $i(0)$ .
2. [15 pts] Analytically derive the capacitor voltage  $v(t)$  for all time instants  $t > 0$ .
3. [10 pts] Intuitively plot the value of  $v(t)$  for all time instants  $t > 0$ . (Remember to indicate the period of oscillation, if any.)
4. [10 pts] What is total energy dissipated by the circuit after time  $t > 0$ ?

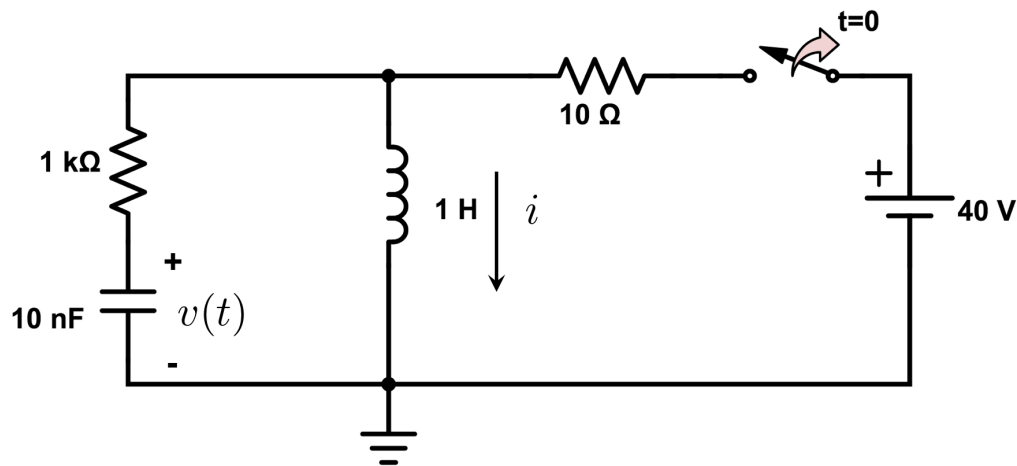


Figure 1