

### Problem 3

Using the impedance method, find  $v_o(t)$ .

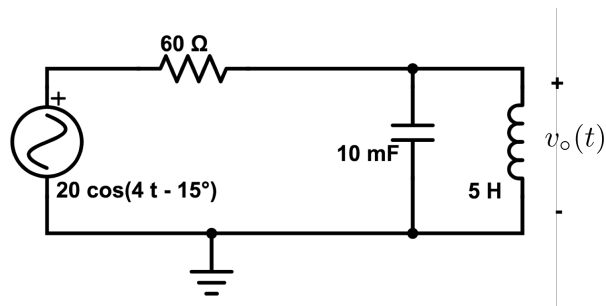


Figure 2