

**Problem 3 (16 points).** A switching circuit has two control inputs (**A** and **B**), two data inputs (**C** and **D**), and one output (**Z**). The circuit performs logic operations on the two data inputs, as shown in this table

<b>A</b>	<b>B</b>	Function performed by this circuit
0	0	OR( <b>C</b> , <b>D</b> )
0	1	AND( <b>C</b> , <b>D</b> )
1	0	XOR( <b>C</b> , <b>D</b> )
0	1	XNOR( <b>C</b> , <b>D</b> )

- (4 points) Use the Shannon's expansion theorem to expand the Boolean function **Z(A,B,C,D)** about variables **A** and **B**.
- (5 points) Use a Karnaugh map to obtain the minimal product of sum (POS) of **Z(A,B,C,D)**.
- (7 points) Convert the above minimal POS to a NAND network, and draw the circuit diagram.